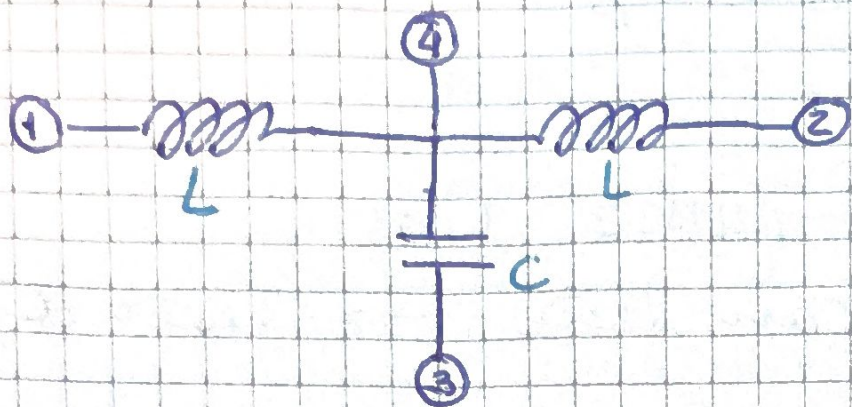



T55

Lucas Gallero.

1er Circuito

$$Y_L = \frac{1}{sL} \quad ; \quad Y_C = sC$$

$$Y_{MAI} = \begin{bmatrix} Y_L & 0 & 0 & -Y_L \\ 0 & Y_L & 0 & -Y_L \\ 0 & 0 & Y_C & -Y_C \\ -Y_L & -Y_L & -Y_C & 2Y_L + Y_C \end{bmatrix}$$

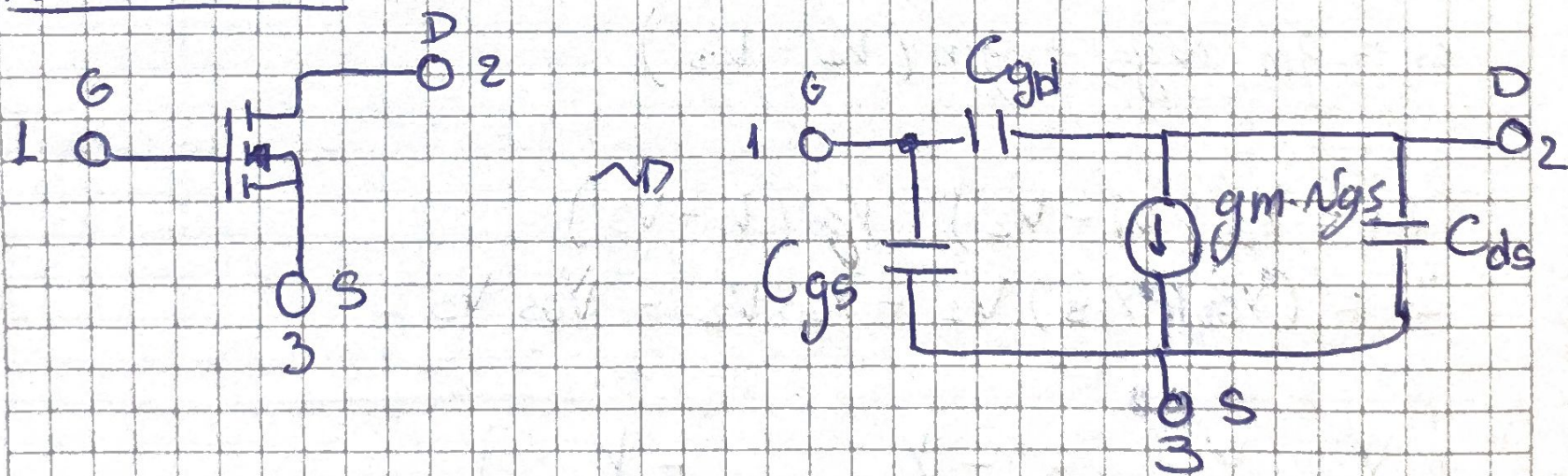2do Circuito

$$C_{gd} = C_{rss} \quad ; \quad C_{gs} = C_{iss} - C_{rss} \quad C_{ds} = C_{oss} - C_{rss}$$

1. Cap. de entrada C_{iss} : Desde gate con Drain y Source puenteados

$$C_{iss} = C_{gs} + C_{gd}$$

2. Cap. Solido C_{oss} : Desde Drain con Gate y Source puenteados

$$C_{oss} = C_{ds} + C_{gd}$$

3. Cap de Transferencia inversa C_{rss}

Es lo que une Drain con Gate $\rightarrow C_{rss} = C_{gd}$.

$$Y_{GD} = sC_{gd} \quad ; \quad Y_{GS} = sC_{gs} \quad ; \quad Y_{DS} = s$$

Nodo 1 $\rightarrow$ Gate Nodo 2 $\rightarrow$ Drain Nodo 3 $\rightarrow$ Source

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{MAG} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$i_m = g_m \cdot v_{gs} = g_m (V_1 - V_3)$$

$$I_1 = Y_{GD} (V_1 - V_2) + Y_{GS} (V_1 - V_3)$$

$$I_1 = (Y_{GD} + Y_{GS}) V_1 - Y_{GD} V_2 - Y_{GS} V_3$$

$$\begin{bmatrix} Y_{GD} + Y_{GS} & -Y_{GD} & -Y_{GS} \end{bmatrix}$$

$$I_2 = Y_{GD} (V_2 - V_1) + Y_{DS} (V_2 - V_3) + g_m (V_1 - V_3)$$

$$I_2 = (g_m - Y_{GD}) V_1 + (Y_{GD} + Y_{DS}) V_2 + (-g_m - Y_{DS}) V_3$$

$$\begin{bmatrix} g_m - Y_{GD} & Y_{GD} + Y_{DS} & -g_m - Y_{DS} \end{bmatrix}$$

$$I_3 = Y_{GS}(V_3 - V_1) + Y_{DS}(V_3 - V_2) - g_m(V_1 - V_3)$$

$$I_3 = (g_m - Y_{GS})V_1 + (-Y_{DS})V_2 + (Y_{GS} + g_m + Y_{DS})$$

$$\begin{bmatrix} -g_m - Y_{GS} & -Y_{DS} & Y_{GS} + g_m + Y_{DS} \end{bmatrix}$$

$$Y_{MAT} = \begin{bmatrix} Y_{GD} + Y_{GS} & -Y_{GD} & -Y_{GS} \\ g_m - Y_{GD} & Y_{GD} + Y_{DS} & -g_m - Y_{DS} \\ -g_m - Y_{GS} & -Y_{DS} & g_m + Y_{GS} + Y_{DS} \end{bmatrix}$$

Con valores de C_{rss} , C_{iss} y C_{oss}

$$Y_{MAT} = \begin{bmatrix} sC_{iss} & -sC_{rss} & -s(C_{iss} - C_{rss}) \\ g_m - sC_{rss} & sC_{oss} & -g_m - s(C_{oss} - C_{rss}) \\ -g_m - s(C_{iss} - C_{rss}) & -s(C_{oss} - C_{rss}) & g_m + s(C_{iss} + C_{oss} - 2C_{iss}) \end{bmatrix}$$

Punto 2

$$Y_{MA1} = \begin{bmatrix} K & 0 & 0 & -K \\ 0 & K & 0 & -K \\ 0 & 0 & K & -K \\ -K & -K & -K & K+2K \end{bmatrix}$$

$$\frac{V_{23}}{V_{13}}$$

$$Y_{(3)} = \begin{bmatrix} K & 0 & -K \\ 0 & K & -K \\ -K & -K & 2K+K \end{bmatrix}$$

$$\frac{V_{23}}{V_{13}} = \frac{C_{12}^{(3)}}{C_{11}^{(3)}}$$

$$C_{11}^{(3)} = \begin{vmatrix} K & -K \\ -K & 2K+K \end{vmatrix} = K(2K+K) - K^2$$

$$C_{11}^{(3)} = 2K^2 + K^2 - K^2 \Rightarrow C_{11}^{(3)} = K^2 + K^2$$

$$C_{12}^{(3)} = (-1)^{1+2} \begin{vmatrix} 0 & -K \\ -K & 2K+K \end{vmatrix} = (-1)^3 (-K^2)$$

$$\Delta = -K^2$$

$$C_{12}^{(3)} = K^2$$

$$\frac{V_{23}}{V_{13}} = \frac{Y_L}{Y_L(Y_L + Y_C)} = \frac{Y_C}{Y_L + Y_C} = \frac{1}{1 + Y_C/Y_L}$$

$$\frac{V_{23}}{V_{13}} = \frac{1}{1 + S^2 LC} = \frac{\frac{1}{LC}}{S^2 + Y_C/Y_L}$$

$$\left[\frac{V_{21}}{V_{31}} \right] = V(1) = \begin{bmatrix} Y_L & 0 & -Y_L \\ 0 & Y_C & -Y_C \\ -Y_L & -Y_C & 2Y_L + Y_C \end{bmatrix}$$

$$\frac{V_{21}}{V_{31}} = \frac{C_{21}^{(1)}}{C_{22}^{(1)}}$$

$$C_{22}^{(1)} = \begin{vmatrix} Y_C & -Y_C \\ -Y_C & 2Y_L + Y_C \end{vmatrix} \rightarrow Y_C(Y_L + Y_C)$$

$$C_{21}^{(1)} = (-1)^{2+1} \begin{vmatrix} 0 & -Y_L \\ -Y_C & 2Y_L + Y_C \end{vmatrix} \rightarrow Y_L Y_C$$

$$\frac{V_{21}}{V_{31}} = \frac{Y_L Y_C}{Y_C(Y_L + Y_C)} = \frac{1}{\frac{Y_C}{Y_L} + 1} = \frac{1}{\frac{1}{S^2 LC} + 1}$$

$$\frac{V_{21}}{V_{31}} = \frac{S^2 LC}{S^2 LC + 1}$$

$$\begin{bmatrix} \frac{V_{12}}{V_{32}} \end{bmatrix} \quad Y^{(2)} = \begin{bmatrix} Y_L & 0 & -Y_L \\ 0 & Y_C & -Y_C \\ -Y_L & -Y_C & 2Y_L + Y_C \end{bmatrix}$$

$$\frac{V_{12}}{V_{32}} = \frac{C_{21}^{(2)}}{C_{22}^{(2)}}$$

$$C_{22}^{(2)} = Y_L (Y_L + Y_C)$$

$$C_{21}^{(2)} = (-1)^{2+1} \cdot Y_L Y_C$$

$$\frac{V_{12}}{V_{32}} = \frac{Y_L Y_C}{Y_L (Y_L + Y_C)} = \frac{Y_C}{Y_L + Y_C} = \frac{1}{\frac{Y_L}{Y_C} + 1}$$

$$\boxed{\frac{V_{12}}{V_{32}} = \frac{S^2 LC}{S^2 LC + 1}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$S^2 LC = -\omega^2 LC = -x^2$$

$$x = \frac{\omega}{\omega_0}$$

$$|T_1| = \frac{1}{|1 - x^2|}$$

$$|T_2| = |T_3| = \frac{|x^2|}{|1 - x^2|} = \frac{x^2}{|1 - x^2|}$$

$$T_1 = \frac{1}{1 - x^2}$$

$$T_2 = \frac{-x^2}{1 - x^2}$$

$$T_1 + T_2 = \frac{1}{1 - x^2} + \frac{-x^2}{1 - x^2} = \frac{1 - x^2}{1 - x^2} = 1$$

Punto 3

$$a) \quad Y_{AA1} = \begin{bmatrix} s(C_{gd} + C_{gs}) & -sC_{gd} & -sC_{gs} \\ g_m - sC_{gd} & s(C_{gd} + C_{ds}) & -g_m - sC_{ds} \\ -g_m - sC_{gs} & -sC_{ds} & g_m + s(C_{gs} + C_{ds}) \end{bmatrix}$$

$$X_{sc} \rightarrow V_s = V_3 = 0$$

$$V_1 = V_g - V_s = V_{13}$$

$$V_2 = V_D - V_s = V_{23}$$

$$Y_{sc} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$Y_{sc} = \begin{bmatrix} s(C_{gd} + C_{gs}) & -sC_{gd} \\ g_m - sC_{gd} & s(C_{gd} + C_{ds}) \end{bmatrix}$$

$$Y_{sc} = \begin{bmatrix} sC_{iss} & -sC_{rss} \\ g_m - sC_{rss} & sC_{oss} \end{bmatrix}$$

$$Y_{DC} \quad V_D = V_2 = 0$$

$$N_1 = N_g - V_d = V_{12}$$

$$N_2 = V_s - V_D = V_{32}$$

$$Y_{DC} = \begin{bmatrix} Y_{11} & Y_{13} \\ Y_{31} & Y_{33} \end{bmatrix}$$

$$Y_{DC} = \begin{bmatrix} s(C_{gd} + C_{gs}) & -sC_{gs} \\ -g_m - s(C_{gs}) & g_m + s(C_{gs} + C_{ds}) \end{bmatrix}$$

$$Y_{DC} = \begin{bmatrix} sC_{iss} & -s(C_{iss} - C_{rss}) \\ -g_m - s(C_{iss} - C_{rss}) & g_m + s(C_{iss} + C_{oss} - 2C_{rss}) \end{bmatrix}$$

b)

$$A = -\frac{Y_{22}}{Y_{21}}$$

$$B = -\frac{1}{Y_{21}}$$

$$C = -\frac{\Delta Y}{Y_{21}}$$

$$D = -\frac{Y_{11}}{Y_{21}}$$

$$\Delta y = (S C_{iss})(S C_{oss}) - (-S C_{rss})(g_m - S C_{rss})$$

$$\Delta y = S^2 C_{iss} C_{oss} + g_m S C_{rss} - S^2 C_{rss}^2$$

$$\Delta y = S g_m C_{rss} + S^2 (C_{iss} C_{oss} - C_{rss}^2)$$

$$T_{sc} = \left[\begin{array}{cc} - \frac{S C_{oss}}{g_m - S C_{rss}} & - \frac{1}{g_m - S C_{rss}} \\ - \frac{S g_m C_{rss} + S^2 (C_{iss} C_{oss} - C_{rss}^2)}{g_m - S C_{rss}} & - \frac{S C_{iss}}{g_m - S C_{rss}} \end{array} \right]$$